
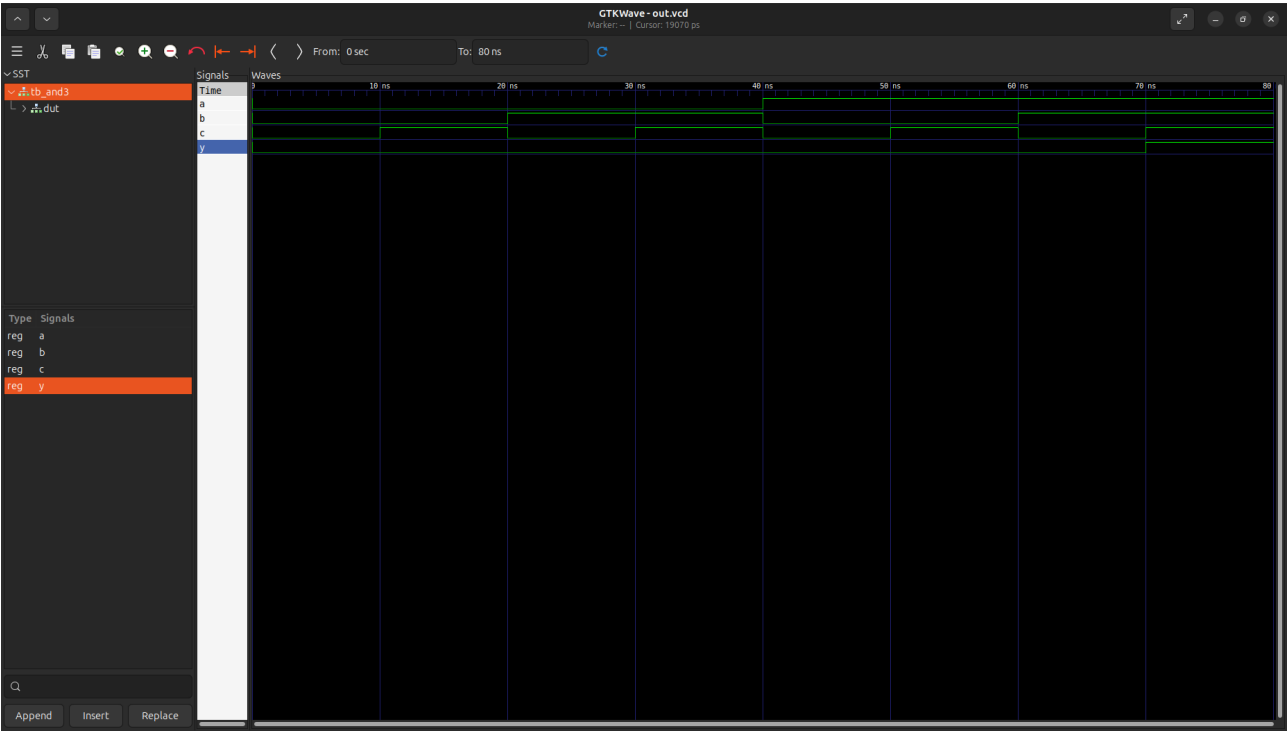


AND3

WAVEFORM

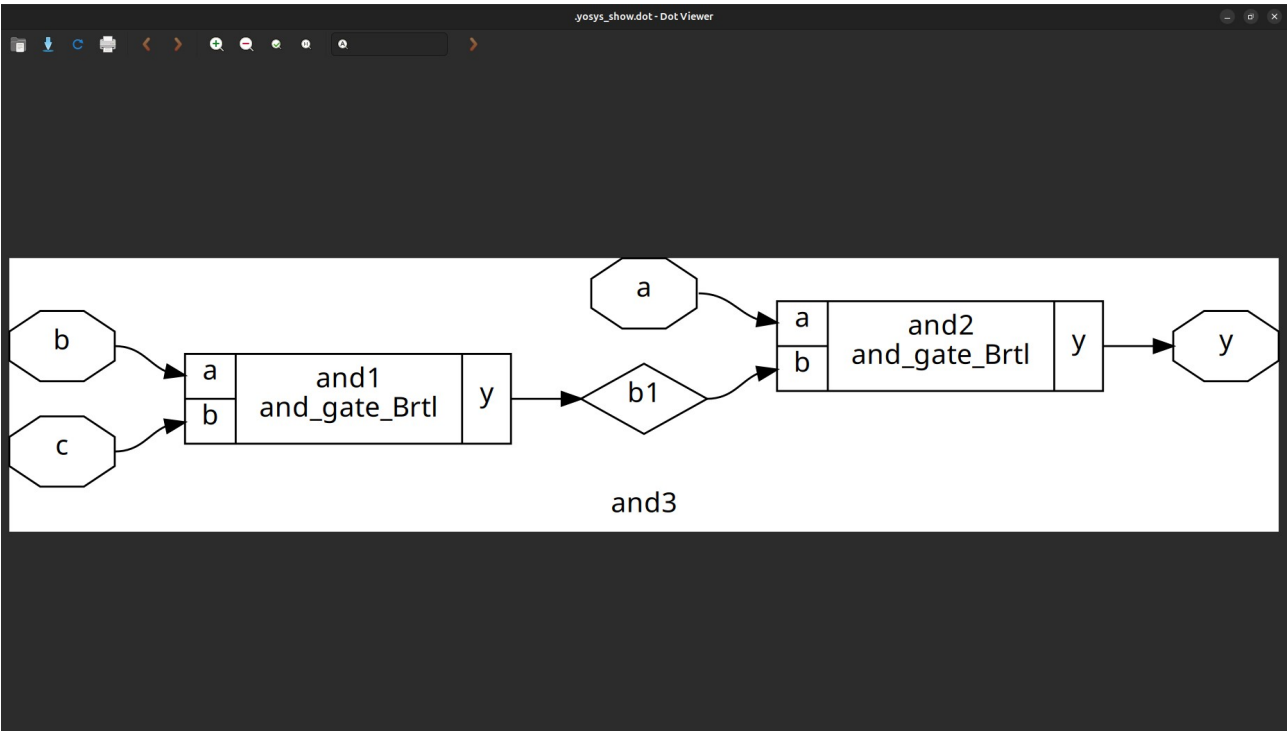


RTL




AND_GATE

WAVEFORM

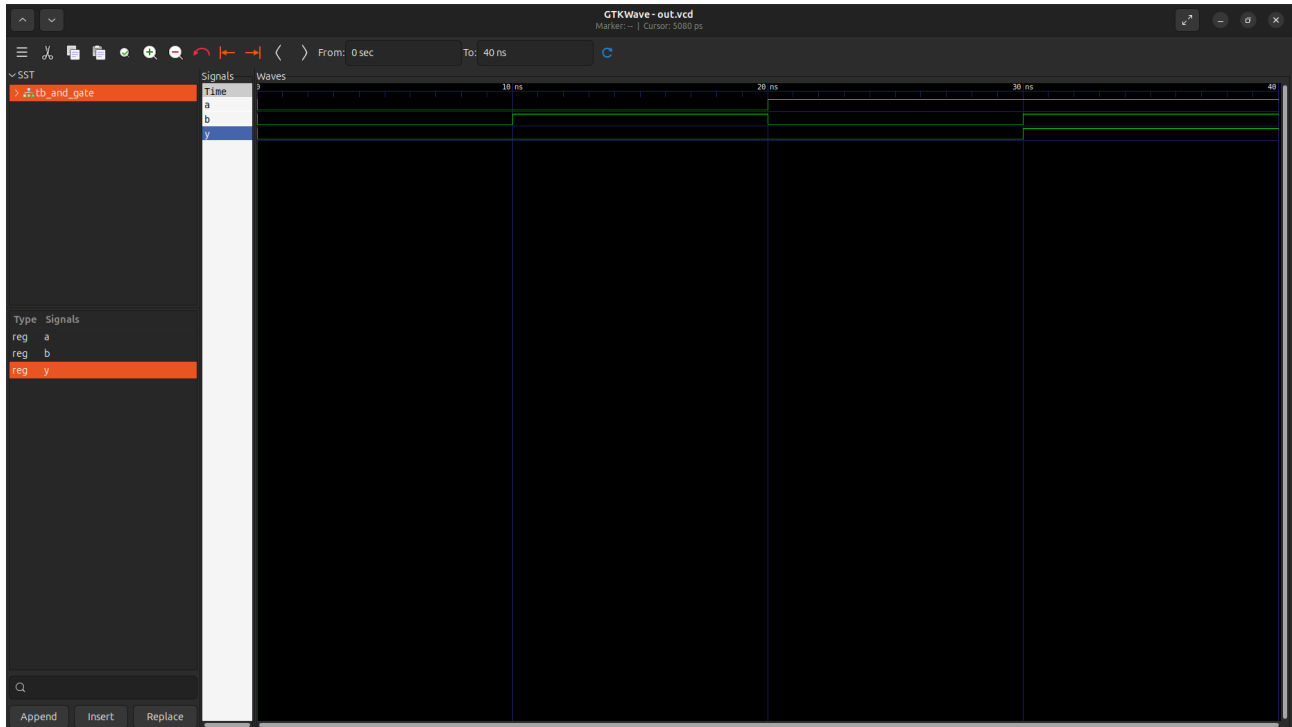


RTL

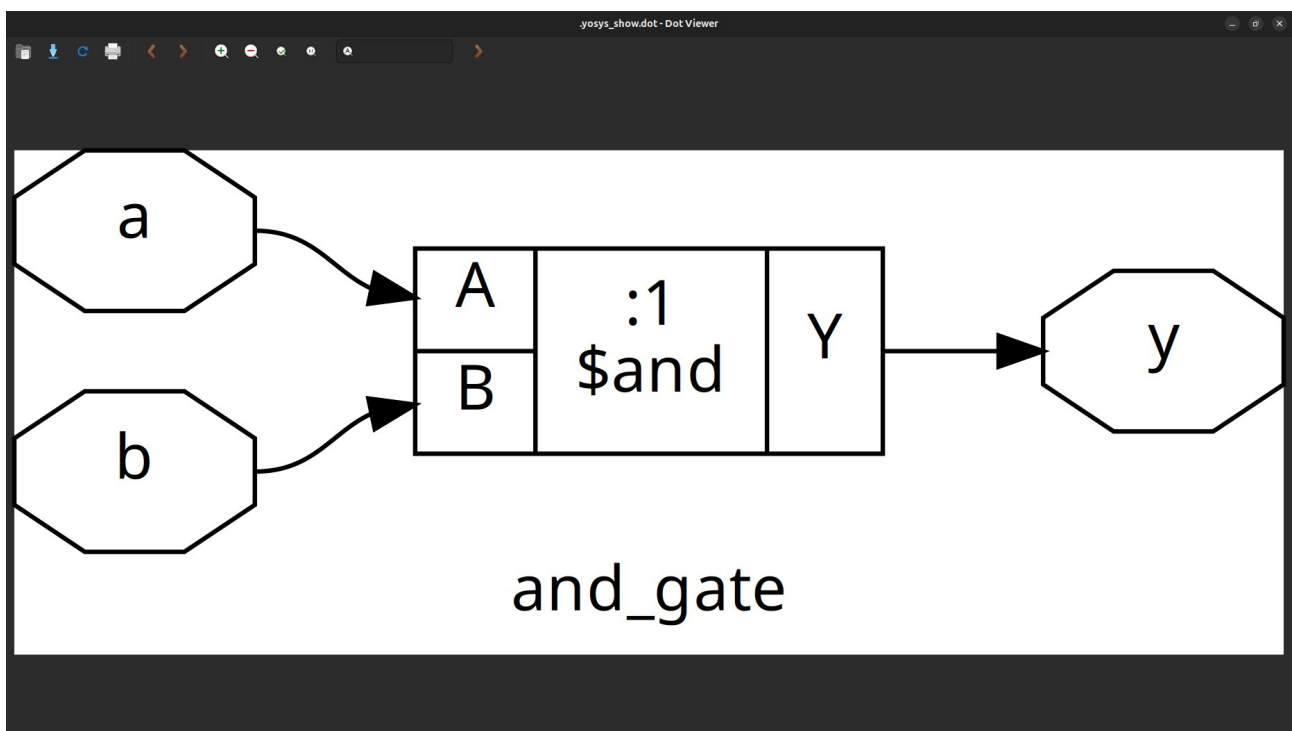


HALF ADDER

WAVEFORM

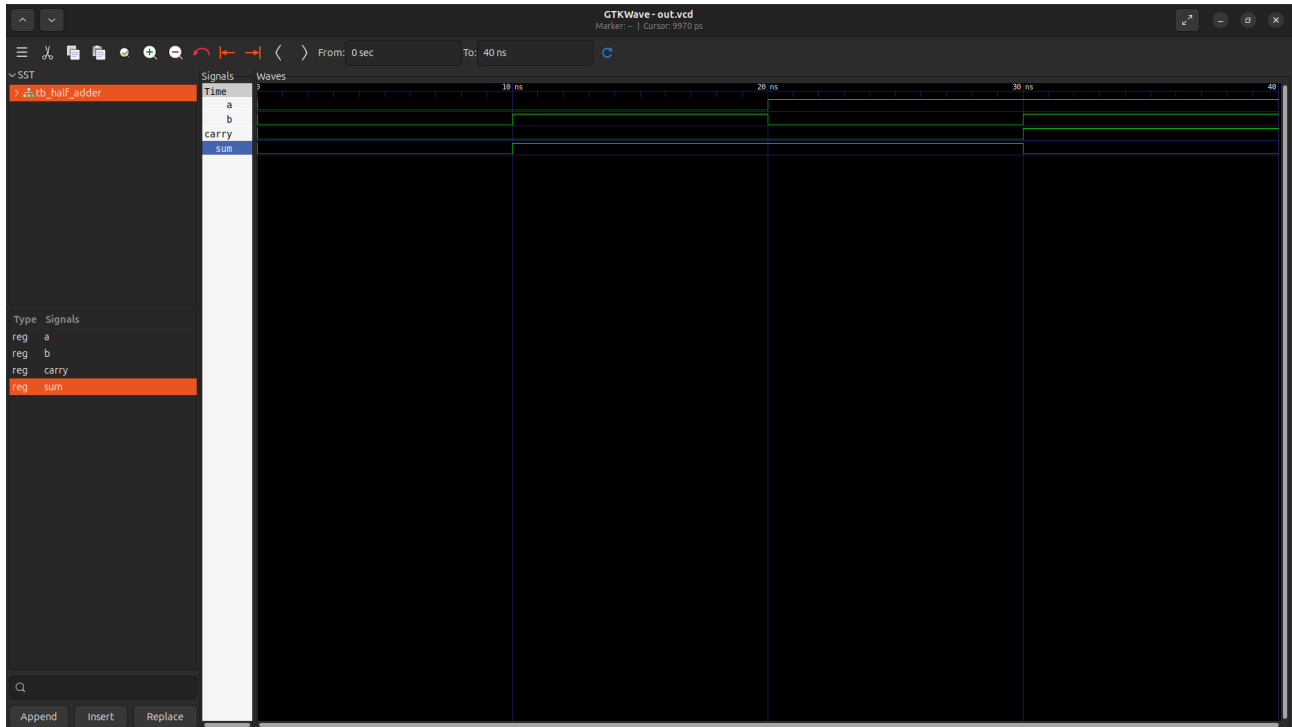


RTL

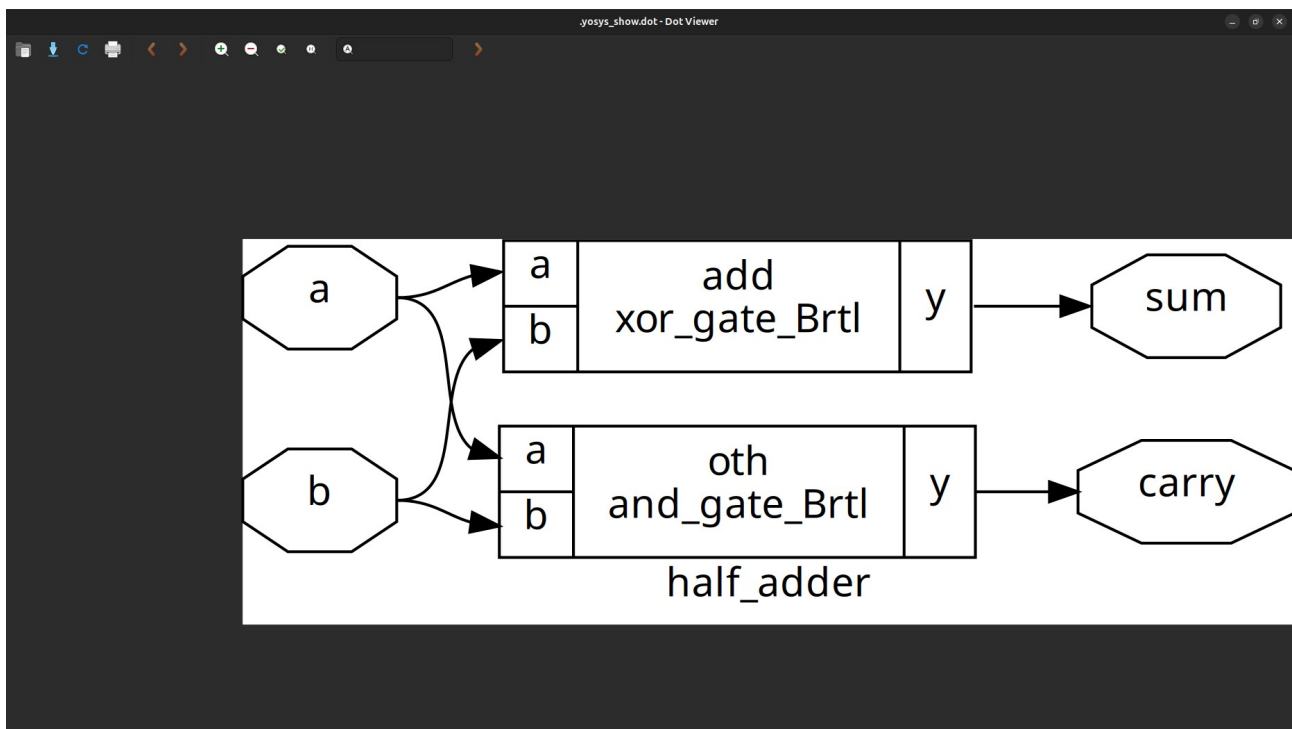


MUX2

WAVEFORM

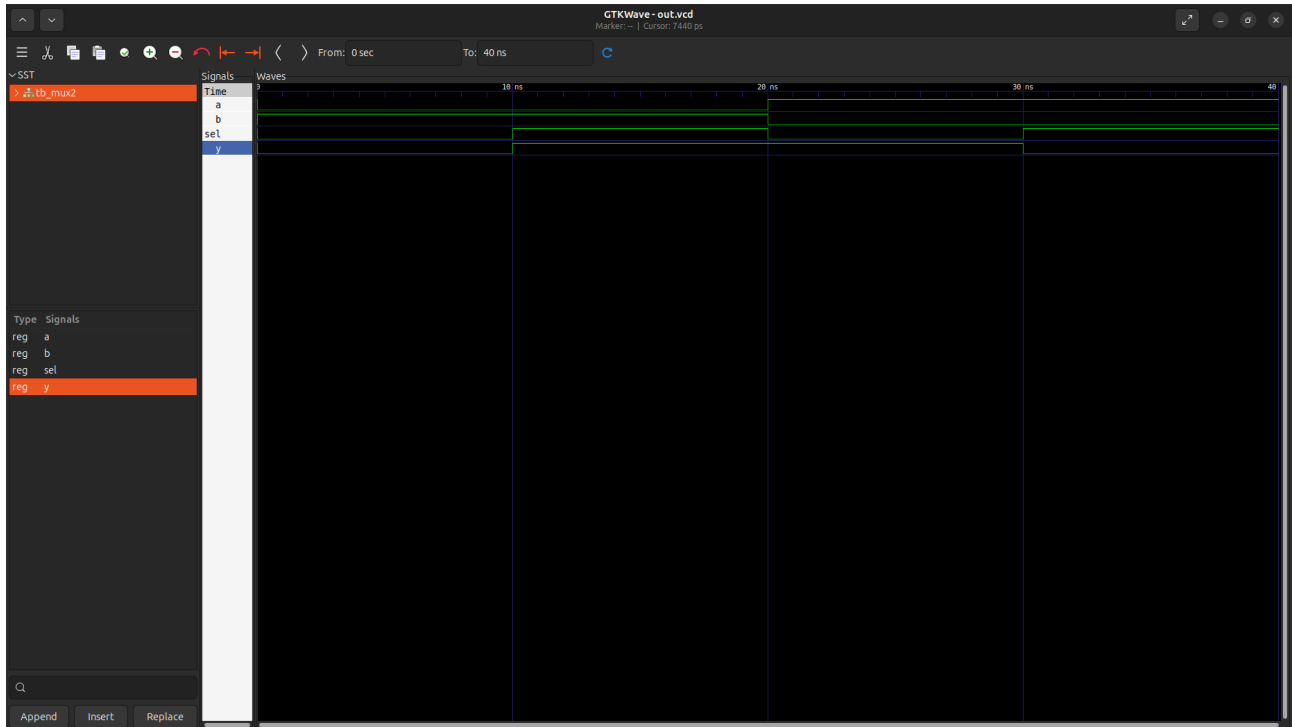


RTL

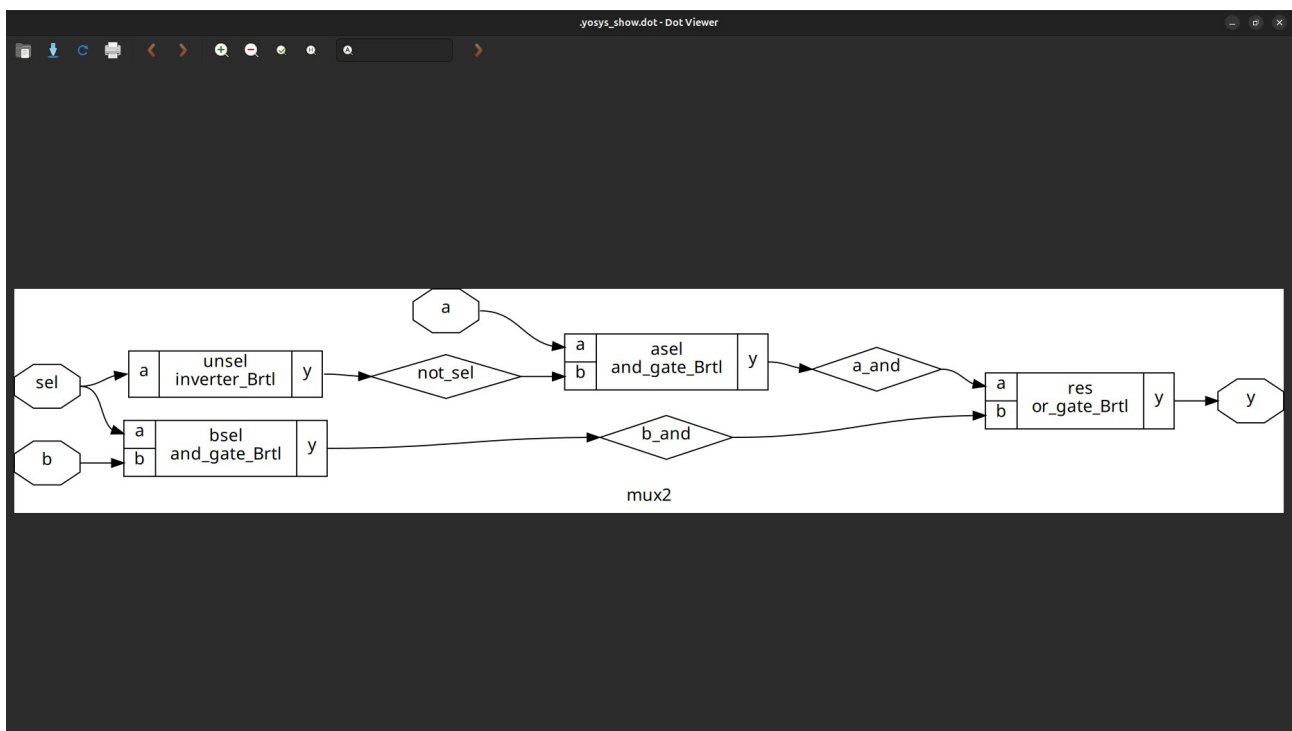


MUX2_EN

WAVEFORM

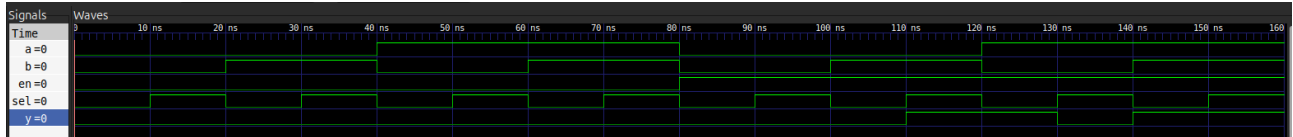


RTL

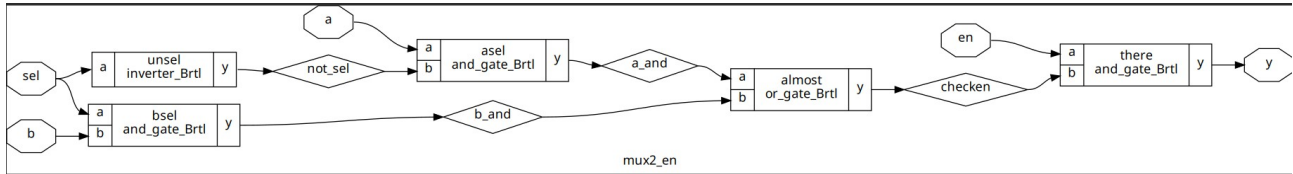

XOR_STRUCTURAL

WAVEFORM

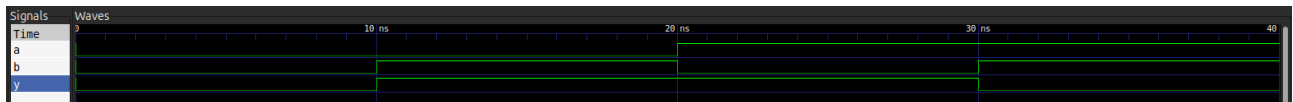

RTL

