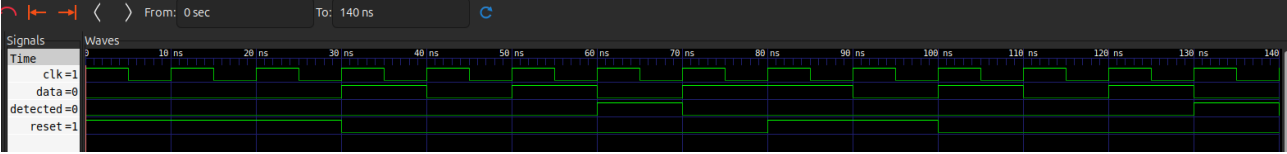


The timing diagram shows the following signal behavior:

- clk**: A periodic square wave signal.
- reset**: A single high pulse at approximately 100 ns.
- coin5**: A pulse at approximately 150 ns.
- coin10**: A pulse at approximately 250 ns.
- dispense**: A pulse at approximately 300 ns.
- change**: A pulse at approximately 350 ns.

The diagram illustrates a vending machine logic circuit. It features a state machine with 16 states (3'000 to 3'111) and a current_state register. The circuit includes a 45-bit multiplexer for the next state, a 7-bit multiplexer for the reset, and a 47-bit shift register for the clock. The output is a 41-bit multiplexer for the change. The diagram is labeled "vending_machine" at the bottom.

SEQ_DET_101_NONOVERLAP
WAVEFORM



RTL

